
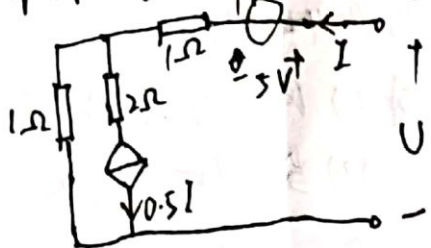


20 ~ 21


1. 求图示电路最简等效电路

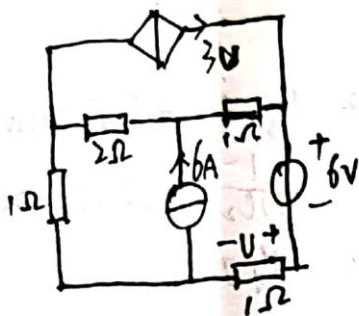


3. 求图示电路中受控源发出的功率



4. 图示电路为电流-电压转换器, 求  $U_o/i_s$

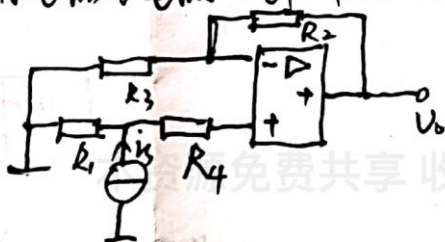

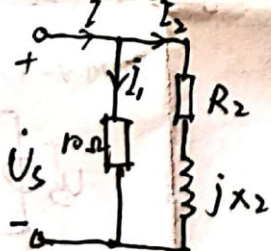
5. 已知  $I_1 = \sqrt{3}A$ ,  $I_2 = I_3 = 1A$ . 以  $U_s$  为参考相量画出图中标出相量, 求  $R_2$  及  $X_2$  的值



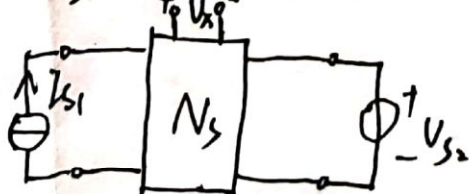
2. 图中  $N_s$  为有源线性三端口网络, 已知  $I_{s1} = 8A$ ,  $U_{s2} = 10V$  时,  $U_x = 10V$ ;

$I_{s1} = -8A$ ,  $U_{s2} = -6V$ ,  $U_x = 22V$ ; 若  $I_{s1} = U_{s2} = 0$  时,  $U_x = 2V$ ;


求  $I_{s1} = 2A$ ,  $U_{s2} = 4V$  时,  $U_x = ?$ .



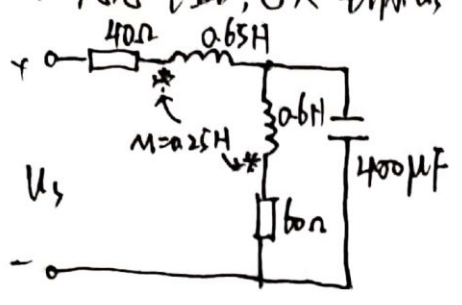
6. 图示正弦稳态电路, 已知电源  $u_s = 500\sqrt{2}\cos 100t$  V, 求其发出的有功功率  $P$  和无功功率  $Q$ .



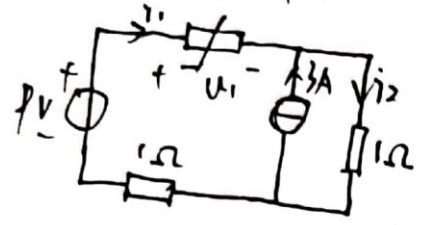
8. 非线性电阻伏安特性为  $u_1 = i_1^2$ . 试求 (1) 静态工作点; (2)  $i_2$ .




9. 写出标准状态方程

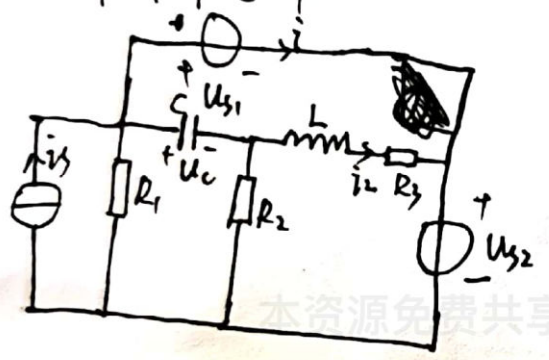

10. 开关断开前电路已达稳态, 试求:  $i_L(0^+)$ ,  $u_C(0^+)$ ,  $\frac{di_L}{dt}|_{0^+}$ ,  $\frac{du_C}{dt}|_{0^+}$ .

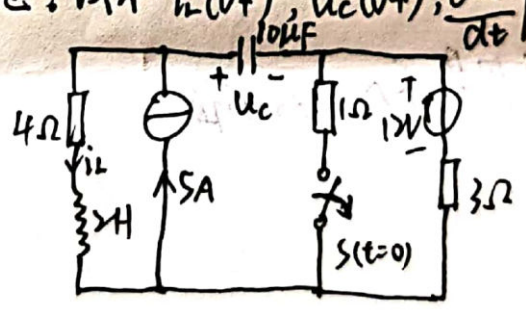

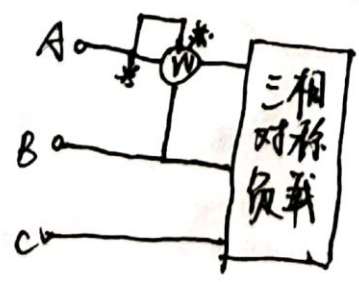7. 图示对称三相电路中, 已知线电压  $U_{AB} = 380$  V, 功率表读数为  $P = 3$  W, 负载功率因数为 0.6. 求: (1) 线电流  $I_A$ ; (2) 负载吸收的总功率.







11.  $N_s$  为线性有源电阻网络,  $R_1=R_2=10\Omega$ , 当  $\beta=1$  时,  $U_{ab}=6V$ ; 当  $\beta=4$  时,  $U_{ab}=8V$ 。

求 (1) 网络  $N_s$  的戴维南等效电路;

(2) 当  $\beta=7$  时,  $U_{ab}$  为多少?

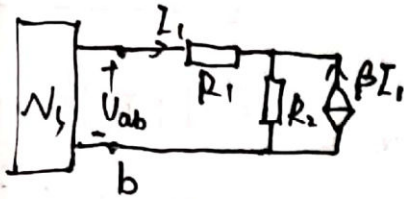


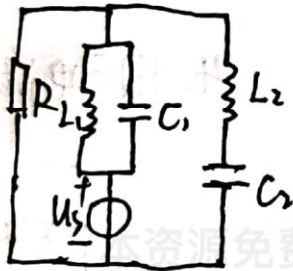12.  $U_s = (150 + 60\sqrt{2}\cos\omega t + 30\sqrt{2}\cos 3\omega t)V$ ,  $\omega L_1 = \frac{1}{\omega C_1} = 2\Omega$ ,  $\omega L_2 = 3\Omega$ ,  $\frac{1}{\omega C_2} = 27\Omega$ ,  $R = 10\Omega$ , 求电容  $C_2$  两端电压有效值及电路消耗的平均功率。




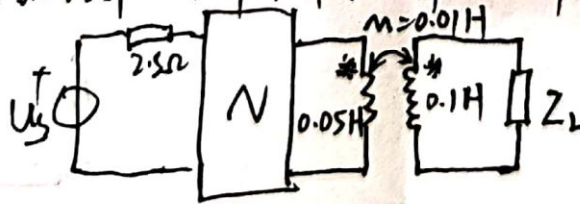13. 若网络  $N$  的  $Y$  参数矩阵为  $Y = \begin{bmatrix} 0.6 & -0.4 \\ -0.4 & 0.6 \end{bmatrix} S$ , 电源电压  $U_s = 20\sqrt{2}\cos 50t V$ 。

求 (1) 负载  $Z_L = 0.5\Omega$  时消耗的平均功率  $P$ ; (2) 若负载  $Z_L$  可变, 则  $Z_L$  为何值时可获得最大功率, 并求此最大功率  $P_{max}$ 。




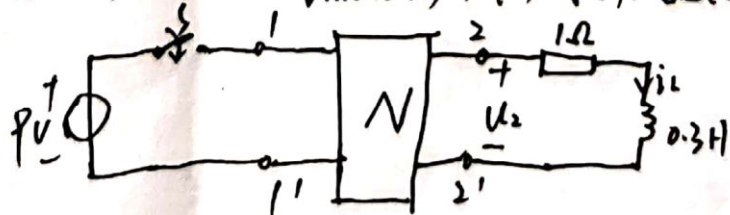
14. 如图所开电源  $U_s$  二端口网络  $N$  的  $R$  参数矩阵为  $\begin{bmatrix} 4 & 2 \\ 2 & 3 \end{bmatrix} \Omega$ ,  $t=0$  时, 开关  $S$  闭合, 闭合前电流  $i_L(0^-) = 1A$ , 求 (1) 闭合后电流  $i_L(t)$ ; (2) 闭合后  $U_2(t)$ 。





2021年电路II (南航)


1: 戴维南 = 最简等效 (戴维南) 诺顿等效

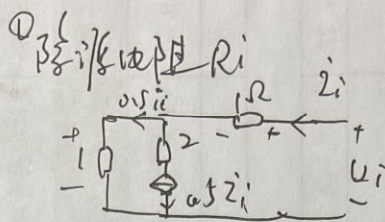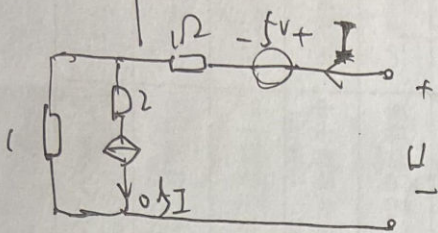

$$0.5i_i + i_i = U_i$$


$$\therefore \frac{U_i}{i_i} = R_i = 15\Omega$$

② 开路电压  $U_0$

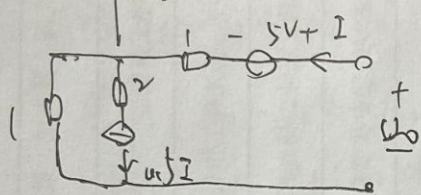

由开路知  $I \Rightarrow$  于是  $U_0 = 5V$

故最简  
诺顿电路

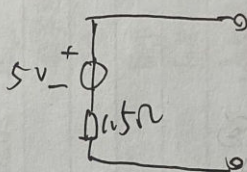

2: 原题为习题册 由表不构设


$$U_x = k_1 I_{s1} + k_2 U_{s2} + k_3$$

$$\begin{cases} 10 = 8k_1 + 10k_2 + k_3 \\ -22 = -8k_1 - 6k_2 + k_3 \\ 2 = 0k_1 + 0k_2 + k_3 \end{cases} \Rightarrow \begin{cases} k_1 = 6 \\ k_2 = -4 \\ k_3 = 2 \end{cases}$$

$$\therefore U_x = 6I_{s1} - 4U_{s2} + 2$$

$$\text{代入 } I_{s1} = 2A; U_{s2} = 4V$$

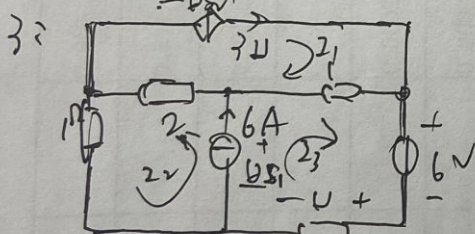
$$\text{可得 } U_x = 2 \times 6 - 4 \times 4 + 2 = -2V$$



$$\begin{cases} U_{s2} + I_2 \times 2 - I_3 = U_{s1} & \text{①} \\ I_2 \times 3 + 2I_1 = U_{s1} & \text{②} \\ I_1 = 3 & \text{③} \\ I_3 \times 2 - 3 \times 1 = U_{s1} - 6 & \text{④} \\ I_3 = 1 & \text{⑤} \\ I_1 + I_3 = 6 & \text{⑥} \end{cases} \Rightarrow \begin{cases} I_1 = 9A \\ I_2 = 9A \\ I_3 = -3A \\ U = -3V \\ U_{s1} = 9V \\ U_{s2} = -6V \end{cases}$$


解 = 由题图设网孔电流  $I_1, I_2, I_3$

由方程组求得  $U_{s2} = -6V$  即  $U = -3V$

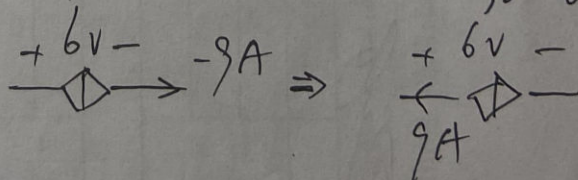

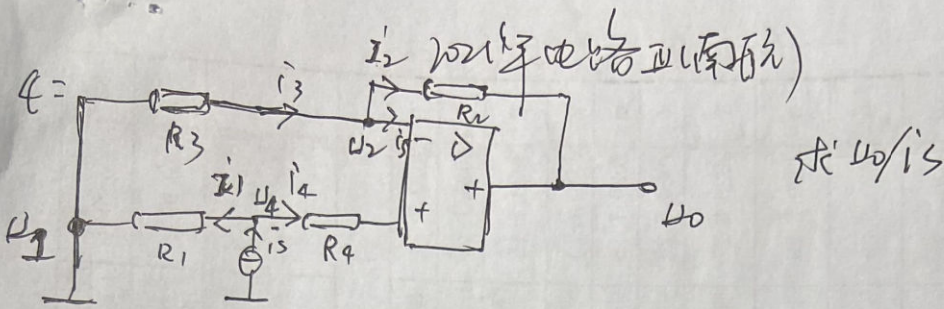该受控源为受控电流源 向外发出功率  $P_{发} = 6 \times 9 = 54W$






解析: 查基本元件的电压电流

由虚短可得  $U_1 = U_4$  ①; 由虚断可得  $i_5 = 0$  ②;  $i_4 = 0$  ③;  $i_3 = i_2$  ④


而  $U_1 = U_4 - i_1 R_1$  ⑤ 故有  $U_2 = U_1 + i_3 R_3$  ⑥  $U_1 = 0$  ⑦

又有  $U_o - U_2 = i_2 R_2$  ⑧ 联立 ①②③④⑤⑥⑦⑧ 可得

$$U_o/i_s = \frac{R_1(R_2 + R_3)}{R_3}$$

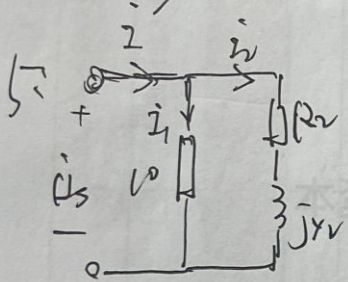

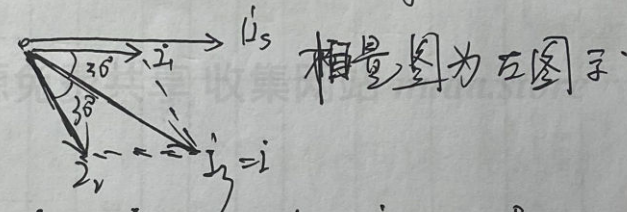由  $i_1, i_2, i_3$  三者关系易得  $i_1, i_2$  呈  $60^\circ$  夹角




而根据图子可得  $U_s = i_1 \cdot 10$  先设  $i_1 = \sqrt{3} \angle 0^\circ \text{ A}$

于是  $U_s = 10\sqrt{3} \angle 0^\circ \text{ V}$  另  $i_2 = 1 \angle 60^\circ \text{ A}$

又有  $U_s = i_2 (R_2 + jX_v) \Rightarrow R_2 + jX_v = \frac{10\sqrt{3} \angle 0^\circ \text{ V}}{1 \angle 60^\circ \text{ A}} = (5\sqrt{3} + 15j) \Omega$

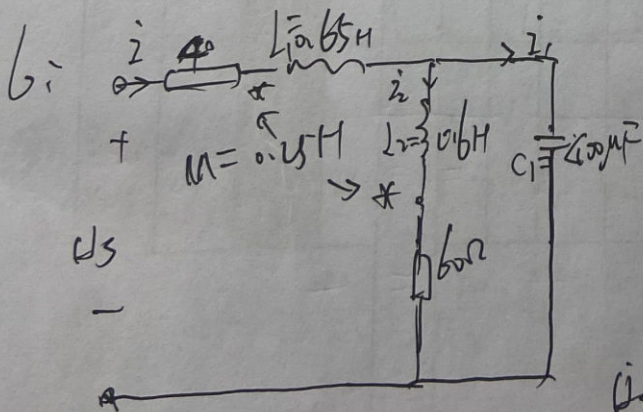$\therefore R_2 = 5\sqrt{3} \Omega; X_v = 15 \Omega$



$jX_1 = j\omega L_1 = j \cdot 65 \Omega; jX_2 = j\omega L_2 = j60 \Omega$   
 $jX_3 = j\omega M = j \cdot 25 \Omega; j\omega C_1 = j \cdot 25 \Omega$

$$\begin{cases} 40i_1 + (j65i_1 - j25i_2) - j25i_1 = U_s & \text{①} \\ (j60i_2 - j25i_1) + 60i_2 = -j25i_1 & \text{②} \\ i_1 + i_2 = i & \text{③} \end{cases} \Rightarrow \begin{cases} i_1 = \frac{U_s}{4}(1-j) \\ i_2 = \frac{U_s}{4}(1-j) \\ i_2 = 0 \end{cases}$$

$U_s = 500 \angle 0^\circ \text{ V}$  而  $i = \frac{U_s}{4}(1-j) \text{ A}$

$\therefore P = 500 \times \frac{U_s}{4} = 3125 \text{ W}; Q = 500 \times (\frac{U_s}{4}) = -3125 \text{ Var}$


[原书答案]



2021 年电路 II (南航)


7: 分析: 考查交流电功率在电路中的流动和功率表的连接

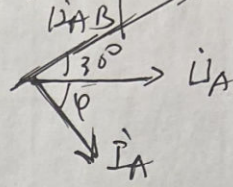(1) 由图可知  $P = U_{AB} \cdot I_A \cdot \cos(\varphi_{\text{电压}} - \varphi_{\text{电流}})$   
 根据相量图  $\varphi_{\text{电压}} - \varphi_{\text{电流}} = 4 + 20^\circ$



代入求得  $I_A = \frac{P}{U_{AB} \cdot \cos(4+20^\circ)} = \frac{27.3}{380 \cdot \cos(53+20^\circ)} = 5.94 \text{ A}$

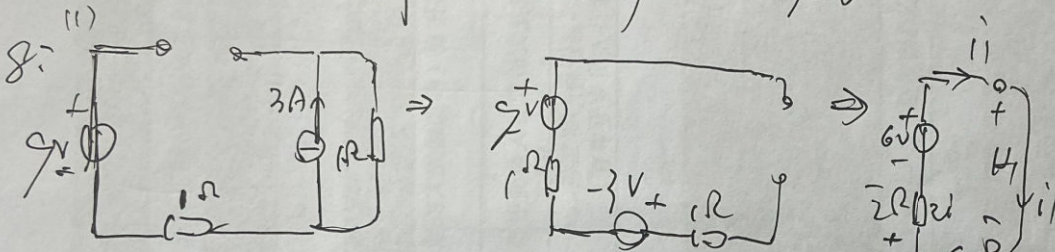
(2) 根据功率计算公式  $P = 3 U_p I_p \cos \varphi = 3 \times \frac{380}{\sqrt{3}} \times 5.94 \times \cos 53^\circ$   
 $\therefore P = \sqrt{3} \times 380 \times 5.94 \times 0.6 = 2346 \text{ W}$



由戴维南定理易得  $u_1 + 2i_1 = 6$  ① 而又得  $u_1 = i_1^2$  ②

联立①②求得  $i_1^2 + 2i_1 - 6 = 0 \Rightarrow i_1 = (-1 + \sqrt{7}) \text{ A}$  (舍负值)

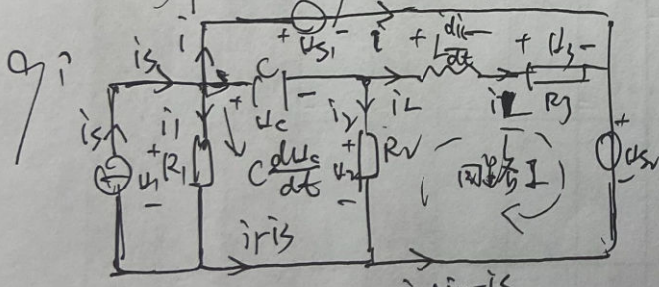(2) 根据  $i_1 = (-1 + \sqrt{7}) \text{ A}$  回到原图求得  $i_2 = 3 + i_1 = 3 - 1 + \sqrt{7} = 2 + \sqrt{7} \text{ A}$




$$\begin{cases} i_1 + i_2 + i_3 = i_s & \text{即 } i_1 + i_2 + C \frac{du_c}{dt} = i_s & \text{①} \\ i_3 = i_2 + i_4 & \text{即 } C \frac{du_c}{dt} = i_2 + i_4 & \text{②} \\ u_2 + u_3 + u_{s2} = u_4 & \text{即 } L \frac{di_L}{dt} + R_3 i_L + u_{s2} = i_2 R_2 & \text{③} \\ u_1 = u_2 + u_4 & \text{即 } i_1 R_1 = u_c + i_2 R_2 & \text{④} \\ u_c + u_1 + u_3 = u_{s1} & \text{即 } u_{s1} = u_c + L \frac{di_L}{dt} + i_1 R_3 & \text{⑤} \\ i_1 = i_2 + i_1 + i_2 - i_3 & \text{即 } i_1 = i_2 - i_4 - i_2 & \text{⑥} \end{cases}$$

联立①②③④⑤ (先由⑤得  $i_2$ ) 然后代入④得  $i_1$  最后代入⑥得  $i_1$  再依次代入①②③

$$\begin{cases} C \frac{du_c}{dt} = \frac{u_{s1}}{R_2} - \frac{u_c}{R_2} + \frac{u_{s2}}{R_2} + i_L \\ L \frac{di_L}{dt} = -u_c + u_{s1} - i_L R_3 \end{cases} \Rightarrow \textcircled{7} \begin{bmatrix} \dot{u}_c \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} -\frac{1}{R_2 C} & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R_3}{L} \end{bmatrix} \begin{bmatrix} u_c \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{1}{R_2 C} & \frac{1}{R_2 C} \\ \frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} u_{s1} \\ u_{s2} \end{bmatrix}$$



2021年电路II (南航)

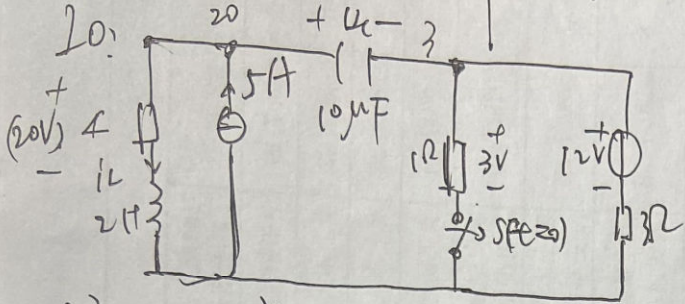


求:  $i_L(0_+), u_C(0_+)$

$$\left. \frac{di_L}{dt} \right|_{0^+}, \left. \frac{du_C}{dt} \right|_{0^+}$$

解: 开关 S 闭合前, 电路处于稳态, 电容电压也不会突变

$$i_L(0_+) = i_L(0_-) = 5A, u_C(0_+) = u_C(0_-) = 1V$$

求  $\left. \frac{di_L}{dt} \right|_{0^+} = u_L(0_+)$  求  $u_L(0_+)$  S 断开之后有新节点电压

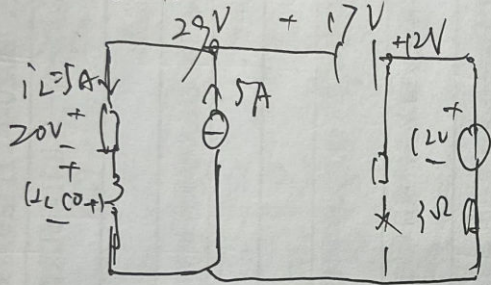


因此由右图可求得

$$u_L(0_+) = 29 - 20 = 9V$$

$$\left. \frac{du_C}{dt} \right|_{0^+} = \frac{u_C(0_+)}{C} = 0 V/s$$

$$\left. \frac{di_L}{dt} \right|_{0^+} = \frac{u_L(0_+)}{L} = 4.5 A/s$$

12:

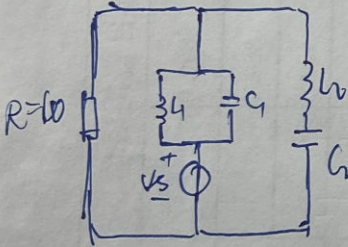

① 直流时: 存在回路, 则 C 端电压  $u_{C(直)} = u_R = 150V$

② 当  $u_S = 60\sqrt{2}\cos\omega t$  时: 有  $\frac{1}{\omega C_1} = \omega L_1$ , 即 C 与 L 串联谐振  
此时所有电压均加载在 L 与 C 串联回路上, 因而相当于开路

即  $u_{C(交)} = 0$

③ 当  $u_S = 30\sqrt{2}\cos\omega t$  时: 有  $\frac{1}{\omega C_2} = \frac{1}{3\omega C_1}$  即 C 与 L 串联谐振

$$Z = \frac{6j \times \frac{2}{3}(-j)}{j6 - \frac{2}{3}j} = -j\frac{3}{4}\Omega \Rightarrow i = \frac{U_S}{Z} = \frac{30\sqrt{2}}{-j\frac{3}{4}} = 40j \text{ (设 } u_S = 30\sqrt{2}\cos\omega t)$$

$$u_{C(交)} = i \cdot \frac{1}{\omega C_2} = 40j \times \frac{2}{3} = 26.7\angle 90^\circ \Rightarrow u_{C(交)} = 26.7V$$

$$u_{C(直)} = 150V$$

因此综合 ②③ 计算可得电容 C 两端电压有效值为  $u_C = \sqrt{u_{C(直)}^2 + u_{C(交)}^2} = \sqrt{150^2 + 26.7^2} \approx 152.5V$



① 直流时  $P_1 = 150W$

② 交流谐振时  $P_2 = 30 \times 40 = 1200W$


$$总功率 P = P_1 + P_2 = 150W + 1200W = 1350W$$



11

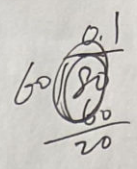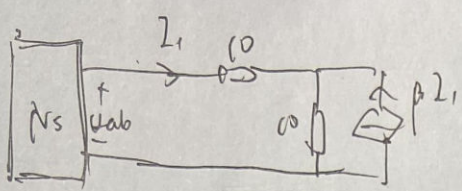

(1)

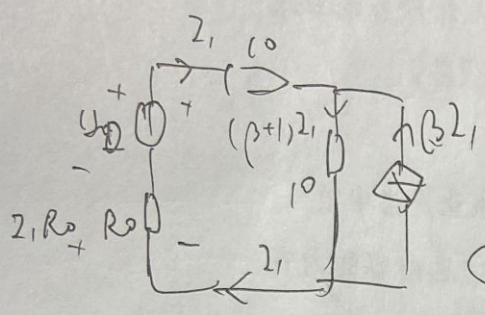

~~有~~  $U_0 - R_0 I_1 = (10 I_1 + 10(\beta+1) I_1)$   
 $U_{ab} = 10 I_1 + 10(\beta+1) I_1$   
 $U_{ab} = (10\beta + 20) I_1$

①  $\beta=1$  时有  $I_1 = \frac{U_{ab}}{10+20} = \frac{6}{30} = 0.2A$


∴  $b = U_0 - R_0 \times 0.2$  ①

②  $\beta=4$  时有  $I_1 = \frac{U_{ab}}{40+20} = \frac{8}{60} = \frac{2}{15}A \Rightarrow 8 = U_0 - \frac{2}{15} R_0$  ②

$\frac{2}{15} R_0 + 8 = 0.2 R_0 + b$

$2 = (0.2 - \frac{2}{15}) R_0 = (\frac{2 \times 15 - 20}{150}) R_0 = \frac{10}{150} R_0 \Rightarrow \begin{cases} U_0 = 12V \\ R_0 = 30\Omega \end{cases}$

故该电路的戴维南电压为  
右图所示

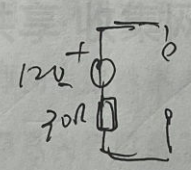

(2)  $\frac{1}{5}\beta \Rightarrow$  时有  $U_0 - R_0 I_1 = (10\beta + 20) I_1 = 90 I_1$


$\begin{cases} U_0 = 12V \\ R_0 = 30\Omega \end{cases}$  代入 得  $12 = 120 I_1 \Rightarrow I_1 = 0.1A \Rightarrow U_0 - R_0 I_1 = U_{ab} = 12 - 3 = 9V$



2021 年电路 II (课程)

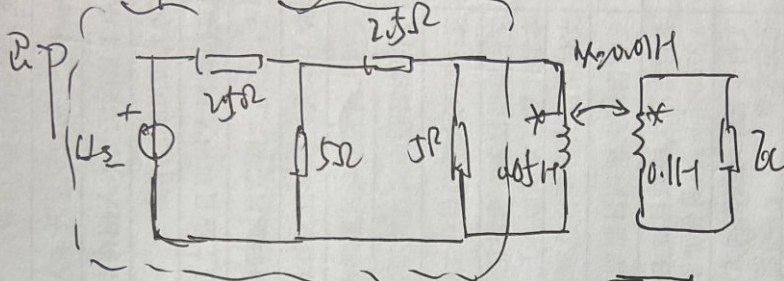13: (1) 根据 \$G\_1\$ 得  $\begin{bmatrix} 0.6 & -0.4 \\ -0.4 & 0.6 \end{bmatrix} \Rightarrow \begin{bmatrix} G_a + G_b & -G_b \\ -G_b & G_b + G_c \end{bmatrix}$

因此该电路为 \$\pi\$ 形等效电路 对应的 \$G\_b = 0.4 \text{ S}\$ \$G\_a = G\_c = 0.2 \text{ S}\$




设  $U_s = 20 \angle 0^\circ \text{ V}$

$\omega = 10$

$$U_{oc} = \frac{\left( \frac{U_s \times 5}{2.5 + 5} \right) \times 5}{2.5 + 5}$$


将电路相内电路等效可得

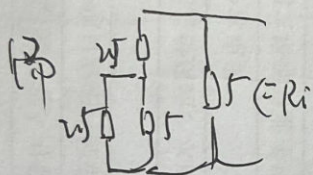

$$R_i = (5 \parallel (5 + 2.5)) \parallel 5 = \frac{\left( \frac{2.5 \times 5}{2.5 + 5} + 2.5 \right) \times 5}{5 + \frac{2.5 \times 5}{2.5 + 5} + 2.5} = \frac{25}{11} \Omega$$

$$U_{oc} = \frac{4}{9} \times 20 \angle 0^\circ \text{ V}$$

即等效为

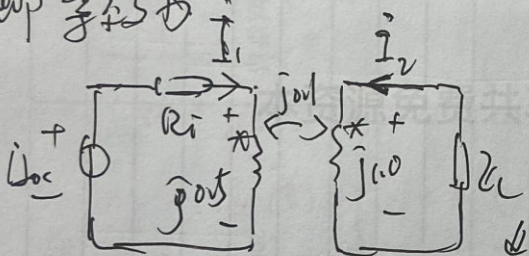

$$\begin{cases} U_{oc} = R_i I_1 + j\omega L_1 I_1 + j\omega M I_2 \\ j\omega L_2 I_2 + j\omega M I_1 = -I_2 Z_L \end{cases}$$

$$\frac{U_{oc} - j\omega M I_2}{R_i + j\omega L_1} \quad j\omega M + j\omega L_2 I_2 = -I_2 Z_L \quad \text{or} \quad \frac{U_{oc} (j\omega M)}{R_i + j\omega L_1} = -I_2 \left( Z_L - \frac{j\omega M}{R_i + j\omega L_1} + j\omega L_2 \right)$$

故最终等效  $U_{oc}'$  为  $U_{oc}' = \frac{U_{oc} (j\omega M)}{R_i + j\omega L_1}$  而  $Z_L' = j\omega L_2 - \frac{j\omega M}{R_i + j\omega L_1}$

(2) 当  $Z_L'$  共轭时 取得最大功率  $P_{max}$  计算  $Z_L'$  因  $U_{oc}$  是含有  $Z_L$  的  
除以 4 倍  $R_i$  即可得到最终结果 即  $P_{max} = \frac{U_{oc}^2}{4R_i}$



解： 2021年电路I (南航)

(1) 使用戴维南等效电路求解原电路为

S 闭合前  $i_L(0^-) = 1A$



(1) 求 S 闭合时对应电流  $i_L(t)$

(2) 求 S 闭合后对应  $U_2(t)$


①

(1) 换路之前  $i_L(0^-) = 1A$

②

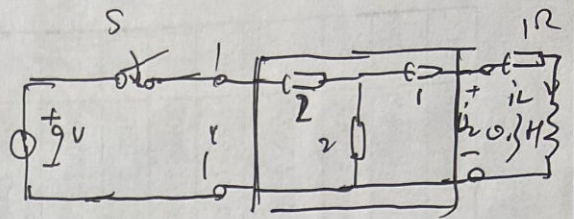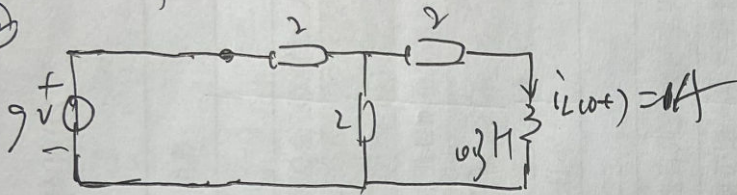


③

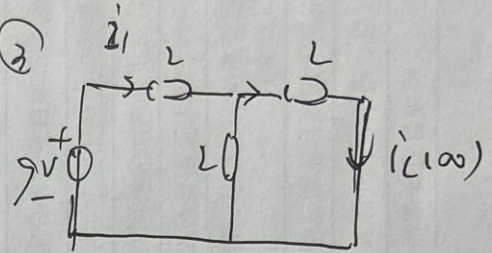

$$I_1 = \frac{9}{3} = 3A \Rightarrow i_L(\infty) = 1.5A$$

④ 求解等效电阻

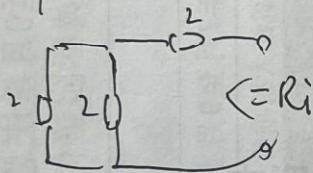

$$\Rightarrow R_i = 2 + 2 \parallel 2 = 2 + 1 = 3\Omega \Rightarrow \tau = \frac{L}{R} = \frac{0.3}{3} = 0.1s$$


⑤ 对应地  $i_L(t) = i_L(\infty) + \{i_L(0^+) - i_L(\infty)\} e^{-\frac{t}{\tau}} = 1.5 + (1 - 1.5)e^{-\frac{t}{0.1}} A$

$$i_L(t) = [1.5 - 0.5e^{-10t}] A$$

(2) 求  $U_2(t)$

① 换路之前  $i_L(0^-) = 1A \Rightarrow U_2(0^-) = 3V$

② 换路之后

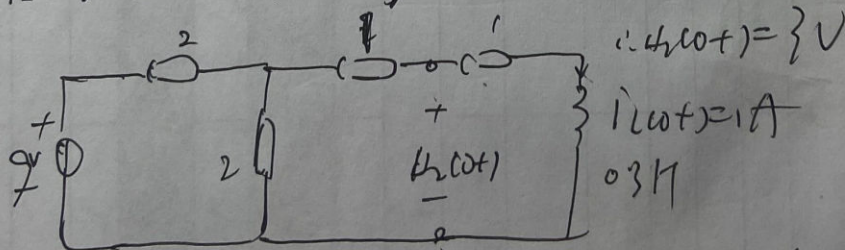

③ 稳定之后  $U_2(\infty) = 1.5V$  ④ 求解等效电阻  $\Rightarrow \tau = \frac{L}{R} = 0.1s$

⑤ 对应地  $U_2(t) = U_2(\infty) + \{U_2(0^+) - U_2(\infty)\} e^{-\frac{t}{\tau}}$

$$U_2(t) = 1.5 + (3 - 1.5)e^{-10t} = [1.5 + 1.5e^{-10t}] V$$